

3-26) The equations for each mass are

$$m_1 \ddot{x}_1 = -b_1 (\dot{x}_1 - \dot{x}_2) - kx_1 + F \cos \omega t$$


$$m_2 \ddot{x}_2 = -b_1 (\dot{x}_2 - \dot{x}_1) - b_2 \dot{x}_2$$

We learned that the analogs of mass, friction, and restoring force are L , R , and $\frac{1}{C}$ respectively. Thus the analogous equations for a circuit are

$$L_1 \ddot{q}_1 + R_1 (\dot{q}_1 - \dot{q}_2) + \frac{1}{C_1} q_1 = V_0 \cos \omega t$$

$$L_2 \ddot{q}_2 + R_1 (\dot{q}_2 - \dot{q}_1) + R_2 \dot{q}_2 = 0$$

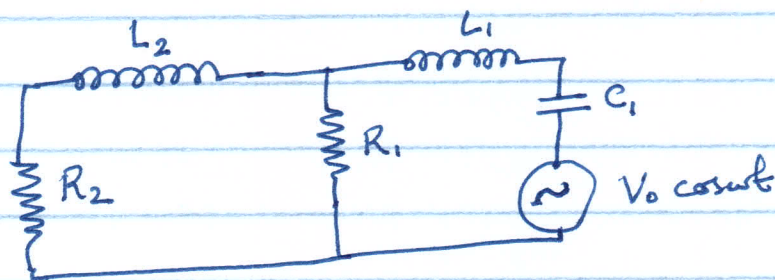Notice that the common term is the $R_1 (I_1 - I_2)$ term, so the circuit is



The impedance seen by the source is

$$\frac{1}{i\omega C_1} + i\omega L_1 + \frac{R_1 (R_2 + i\omega L_2)}{R_1 + R_2 + i\omega L_2}$$